


# שפת תכנון חומרה ורילוג - Verilog

**Verilog – Finite State Machine (FSM)**

Dr. Avihai Aharon

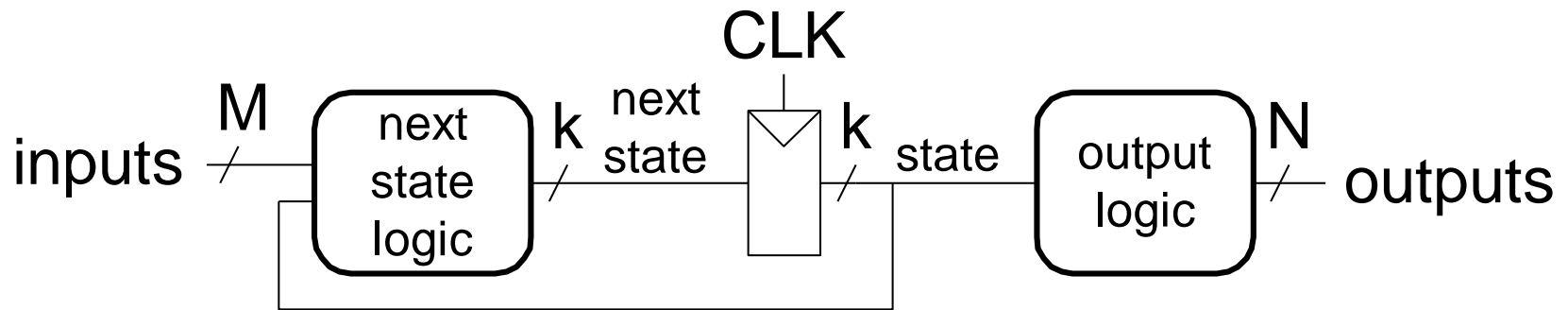
# Finite State Machines (FSMs)

- **Each FSM consists of three separate parts:**
  - next state logic
  - state register
  - output logic


 
# FSM Example: Divide by 3

- Output should be “1” every 3 clock cycles
  - state S0



# FSM in Verilog - Definitions

```
module divideby3FSM (input clk,  
                    input reset,  
                    output q);  
  
    reg [1:0] state, nextstate;  
  
    parameter S0 = 2'b00;  
    parameter S1 = 2'b01;  
    parameter S2 = 2'b10;
```

- We define state and nextstate as 2-bit reg
- The parameter descriptions are optional, it makes reading easier

# FSM in Verilog - State Register

```
// state register
always @ (posedge clk, posedge reset)
    if (reset) state <= S0;
    else      state <= nextstate;
```

- This part defines the state register (memorizing process)
- Sensitive to only clk, reset
- In this example reset is active when '1'

# FSM in Verilog - Next State Calculation

```
// next state logic
always @ (*)
  case (state)
    S0:      nextstate = S1;
    S1:      nextstate = S2;
    S2:      nextstate = S0;
    default: nextstate = S0;
  endcase
```

- Based on the value of state we determine the value of nextstate
- An always .. case statement is used for simplicity.

# FSM in Verilog - Output Assignments

```
// output logic  
assign q = (state == S0);
```

- In this example, output depends only on state
  - Moore type FSM
- We used a simple combinational assign

# FSM in Verilog – Full code

```
module divideby3FSM (input clk, input reset, output q);  
    reg [1:0] state, nextstate;
```


```
    parameter S0 = 2'b00;  
    parameter S1 = 2'b01;  
    parameter S2 = 2'b10;
```

```
    always @ (posedge clk, posedge reset) // state register  
        if (reset) state <= S0;  
        else state <= nextstate;
```

```
    always @ (*)  
        case (state)  
            S0:    nextstate = S1;  
            S1:    nextstate = S2;  
            S2:    nextstate = S0;  
            default: nextstate = S0;  
        endcase
```



```
    assign q = (state == S0);  
endmodule
```

// next state logic

 



# Parity checker – Mealy FSM

 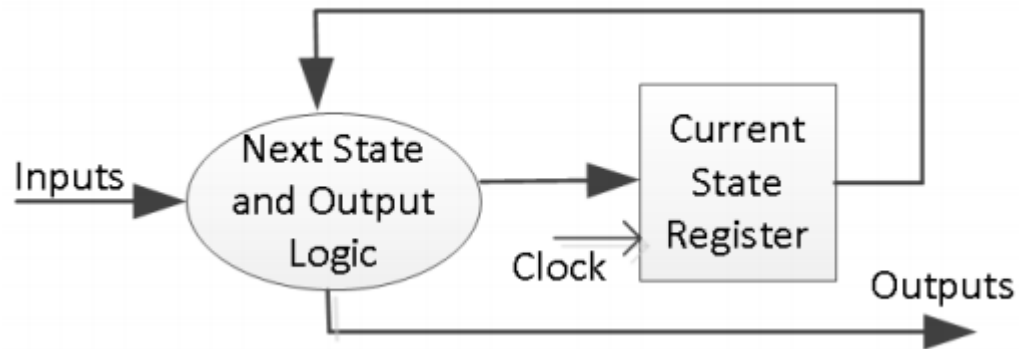

# Parity checker – Mealy FSM

```
module mealy_2processes(input clk, input reset, input x, output reg parity);
    reg state, nextstate;
    parameter S0=0, S1=1;



    always @(posedge clk or posedge reset)    // always block to update state
    if (reset)
        state <= S0;
    else
        state <= nextstate;

    always @(state or x) // always block to compute both output & nextstate
    begin
        parity = 1'b0;
        case(state)
            S0: if(x)
                begin
                    parity = 1; nextstate = S1;
                end
                else
                    nextstate = S0;
            S1: if(x)
                nextstate = S0;
                else
                    begin
                        parity = 1; nextstate = S1;
                    end
            default:
                nextstate = S0;
        endcase
    end
endmodule
```

# Parity checker – Mealy FSM

```
module mealy_3processes(input clk, input reset, input x, output reg parity);  
    ■  
    ■  
    ■  
  
    always @(state or x) // always block to compute output  
    begin  
        parity = 1'b0;  
        case(state)  
            S0: if(x)  
                parity = 1;  
            S1: if(!x)  
                parity = 1;  
        endcase  
    end  
    always @(state or x) // always block to compute nextstate  
    begin  
        nextstate = S0;  
        case(state)  
            S0: if(x)  
                nextstate = S1;  
            S1: if(!x)  
                nextstate = S1;  
        endcase  
    end  
end  
endmodule
```

# Parity checker – Moore FSM

 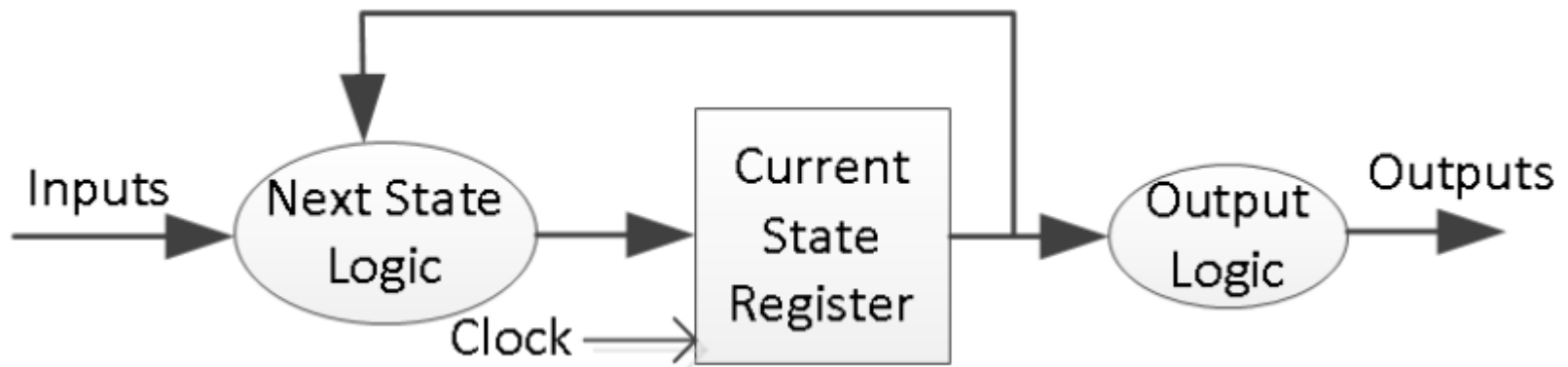

# Parity checker – Moore FSM

```
module moore_3processes(input clk, input reset, input x, output reg parity);
    reg state, nextstate;
    parameter S0=0, S1=1;

    always @(posedge clk or posedge reset) // always block to update state
    if (reset)
        state <= S0;
    else
        state <= nextstate;

    always @(state) // always block to compute output
    begin
        case(state)
            S0: parity = 0;
            S1: parity = 1;
        endcase
    end

    always @(state or x) // always block to compute nextstate
    begin
        nextstate = S0;
        case(state)
            S0: if(x)
                    nextstate = S1;
            S1: if(!x)
                    nextstate = S1;
        endcase
    end
end
endmodule
```

# FSM Moore template

```
module moore_regular_template
(
    input clk, reset,
    input [<size>] input1, input2, ...,
    output reg [<size>] output1, output2, ...,
);

    parameter [<size_state>] // for 4 states : size_state = 1:0
    s0 = 0,
    s1 = 1,
    s2 = 2,
    ... ;

    reg[<size_state>] present_state, next_state;

// state register : present_state
// This process contains sequential part and all the D-FF are
// included in this process. Hence, only 'clk' and 'reset' are
// required for this process.
always @(posedge clk, posedge reset) begin
    if (reset) begin
        present_state <= s0;
    end
    else begin
        present_state <= next_state;
    end
end
end
```

# FSM Moore template

```
// next state logic : next_state
// This is combinational of the sequential design,
// which contains the logic for next-state
// include all signals and input in sensitive-list except next_state
always @(input1, input2, ..., present_state) begin
    case (present_state)
        s0 : begin
            if (<condition>) begin // if (input1 = 2'b01) then
                next_state = s1;
            end
            else if (<condition>) begin // add all the required conditionstion
                next_state = ...;
            end
            else begin // remain in current state
                next_state = s0;
            end
        end
        s1 : begin
            if (<condition>) begin // if (input1 = 2'b10) then
                next_state = s2;
            end
            else if (<condition>) begin // add all the required conditionstions
                next_state = ...;
            end
            else begin // remain in current state
                next_state = s1;
            end
        end
        s2 : begin
            ...
        end
    endcase
end
```

# FSM Moore template

```
// combination output logic
// This part contains the output of the design
// no if-else statement is used in this part
// include the present_state in sensitive-list in moore FSM
always @(present_state) begin
    // default outputs
    output1 = <value>;
    output2 = <value>;
    ...
    case (present_state)
        s0 : begin
            output1 = <value>;
            output2 = <value>;
            ...
        end
        s1 : begin
            output1 = <value>;
            output2 = <value>;
            ...
        end
        s2 : begin
            ...
        end
    endcase
end
```

```
// optional D-FF to remove glitches
always @(posedge clk, posedge reset)
begin
    if (reset) begin
        new_output1 <= ... ;
        new_output2 <= ... ;
    end
    else begin
        new_output1 <= output1;
        new_output2 <= output2;
    end
end

endmodule
```



# TB - for loop

```
module TB ();  
.  
.  
Parameter data = 10'b0011101100;  
Integer i;  
.  
.  
initial  
begin  
.  
.  
.  
    for(i=0; i<10; i=i+1)  
    begin  
        x = data[i];  
        # 20  
    end  
.  
.  
endmodule
```

# Fibonacci Calculator

- $F(0) = 0, F(1) = 1$
- $F(n) = F(n - 1) + F(n - 2)$ , when  $n > 1$
- Examples:

$F_0$	$F_1$	$F_2$	$F_3$	$F_4$	$F_5$	$F_6$	$F_7$	$F_8$	$F_9$
0	1	1	2	3	5	8	13	21	34

# Fibonacci Calculator

- Design a FSM with the interface below.
- input\_s is “n”, and fibo\_out is “F(n)”.
- Wait in IDLE state until begin\_fibo.
- When testbench sees done==1, it will check if fibo\_out== F(input\_s).

```
module fibonacci_calculator (input clk, reset_n,  
                             input [4:0] input_s,  
                             input begin_fibo,  
                             output [15:0] fibo_out,  
                             output done);
```

```
...
```


```
always @(posedge clk, negedge reset_n)
```

```
begin
```

```
...
```

```
end
```

```
endmodule
```

 

# Fibonacci Calculator

- Basic idea is to introduce 3 registers:

```
reg [4:0] counter;
```

```
reg [15:0] R0, R1;
```

- Set loop counter to “n”

```
counter = input_s;
```

- Repeat as long as counter is greater than 1  
since we already know what F(0) and F(1) are:

```
counter = counter - 1;
```

```
R1 = R1 + R0;
```

```
R0 = R1;
```

- Finally, set output to “F(n)”

```
done = 1;
```

```
fibonacci_out = R0;
```

# Fibonacci Calculator

```
module fibonacci_calculator (input clk, reset_n,  
                             input [4:0] input_s,  
                             input begin_fibo,  
                             output [15:0] fibo_out,  
                             output done);  
  
    parameter IDLE=2'b00, COMPUTE=2'b01, DONE=2'b10;  
    reg [1:0] state, Nxt_state;  
  
    reg [4:0] count;  
    reg [15:0] R1, R0;  
  
    //state register  
    always @(posedge clk, negedge reset_n)  
    begin  
        if (!reset_n)  
            state <= IDLE;  
        else  
            state <= Nxt_state;  
        end  
  
    // output logic  
    assign done = (state== DONE);  
    assign fibo_out = (state== DONE)? R1 : 16'd0;
```

21

```
    // nextstate logic  
    always @(*)  
    case (state)  
        IDLE:  
            if (begin_fibo) begin  
                count = input_s;  
                R1 = 1;  
                R0 = 0;  
                Nxt_state = COMPUTE;  
            end  
        else  
            Nxt_state = IDLE;  
  
        COMPUTE:  
            if (count > 1) begin  
                count = count - 1;  
                R1 = R1 + R0;  
                R0 = R1;  
                Nxt_state = COMPUTE;  
            end else begin  
                Nxt_state = DONE;  
            end  
  
        DONE:  
            Nxt_state <= IDLE;  
    endcase  
endmodule
```