

שפת תכנון חומרה ורילוג - Verilog


Verilog – Asynchronous Modules

Dr. Avihai Aharon

Asynchronous Counter

- 4-bit asynchronous counter; Ripple counter. This is a simple counter without reset or load options.
 
```
module counter( clk, count );  
input clk;  
output[3:0] count;  
  
reg[3:0] count;  
wire clk;  
initial  
    count = 4'b0;  
  
always @( negedge clk )  
    count[0] <= ~count[0];  
  
always @( negedge count[0] )  
    count[1] <= ~count[1];  
  
always @( negedge count[1] )  
    count[2] <= ~count[2];  
  
always @( negedge count[2] )  
    count[3] <= ~count[3];  
endmodule
```



Asynchronous Counter (electroSofts.com)

Asynchronous Counter

```

module ripple ( input clk,
                input rstn,
                output [3:0] out);

  wire q0;
  wire qn0;
  wire q1;
  wire qn1;
  wire q2;
  wire qn2;
  wire q3;
  wire qn3;

  dff dff0 ( .d (qn0),
             .clk (clk),
             .rstn (rstn),
             .q (q0),
             .qn (qn0));


  dff dff1 ( .d (qn1),
             .clk (q0),
             .rstn (rstn),
             .q (q1),
             .qn (qn1));

  dff dff2 ( .d (qn2),
             .clk (q1),
             .rstn (rstn),
             .q (q2),
             .qn (qn2));

  dff dff3 ( .d (qn3),
             .clk (q2),
             .rstn (rstn),
             .q (q3),
             .qn (qn3));

  assign out = {qn3, qn2, qn1, qn0};
endmodule

```

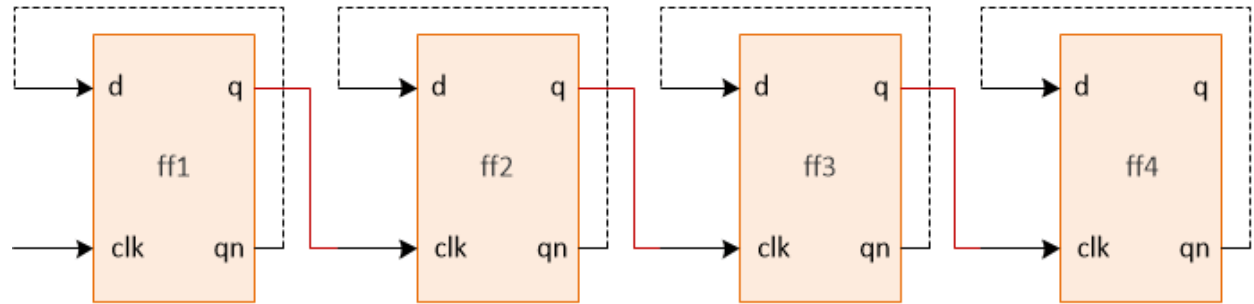

```

module dff (input d,
            input clk,
            input rstn,
            output reg q,
            output qn);
  always @ (posedge clk or negedge rstn)
    if (!rstn)
      q <= 0;
    else
      q <= d;


  assign qn = ~q;
endmodule

```

UART (Universal Asynchronous Receiver Transmitter)

UART, Serial Port, RS-232 Interface

UART Serial Data Stream:

 

The baud rate is the rate at which the data is transmitted. For example, 9600 baud means 9600 bits per second.

UART parameters:

Baud Rate	(9600, 19200, 115200, others)
Number of Data Bits	(7, 8)
Parity Bit	(On, Off)
Stop Bits	(0, 1, 2)